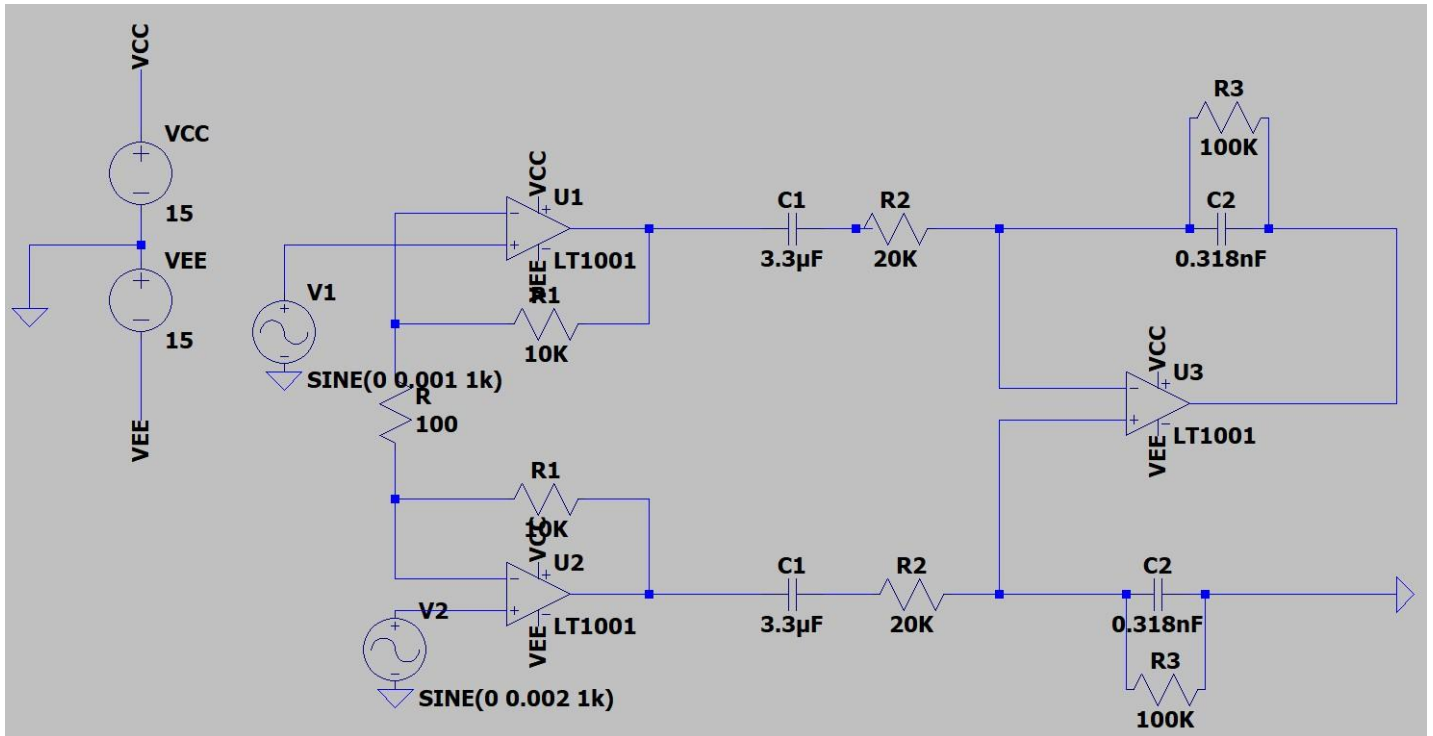


A High Gain and High CMRR Instrumentation Amplifier for Biomedical Applications

CIRCUIT DIAGRAM



DESIGN:

$$G = \left(1 + \frac{2R1}{Rg}\right) \left(\frac{R3}{R2}\right)$$

For Gain of **1000**,

Choose the resistor values as **R1 =10k Ω , R2 =20K Ω , R3=100K Ω , Rg=100 Ω**

(By changing Rg, we can achieve desired Gain)

- Gain of First , 2 opamplifiers (act like buffer)

$$A_v = \left(1 + \frac{2R1}{R2}\right) = 201$$

- C1:** C1 blocks the dc offset at the input act as a short circuit (Forms a High pass Filter (**HPF**))

To allow low frequency AC signal impedance of capacitance C1,

$$Z_{c1} \leq 0.01 R1 = 0.01 * (10K) = 100 \Omega$$

$$C1 = \frac{1}{2\pi f Z_{C1}} = \frac{1}{2\pi (1k * 100)} = 3.3 \mu F$$

- **C2:** C2 suppresses the noise at high frequency (In this case **5kHz**)

$$C2 = \frac{1}{2\pi f R3} = \frac{1}{2\pi (5k * 100k)} = 0.318 nF$$

CMRR

$$CMRR = 20 \log \frac{A_d}{A_{cm}} = 20 \log \frac{1000}{0.001} = 120 dB$$

ADVANTAGES

High CMRR: Rejects noise from power lines and other interference sources, critical for biomedical signals.


High Gain: Amplifies weak biomedical signals like ECG or EEG.

Offset Elimination: Input capacitors block DC offsets, maintaining signal integrity.

Stability: Feedback capacitors improve high-frequency stability and reduce noise.

SIMULATION RESULTS

Input Wave forms (V1 , V2)

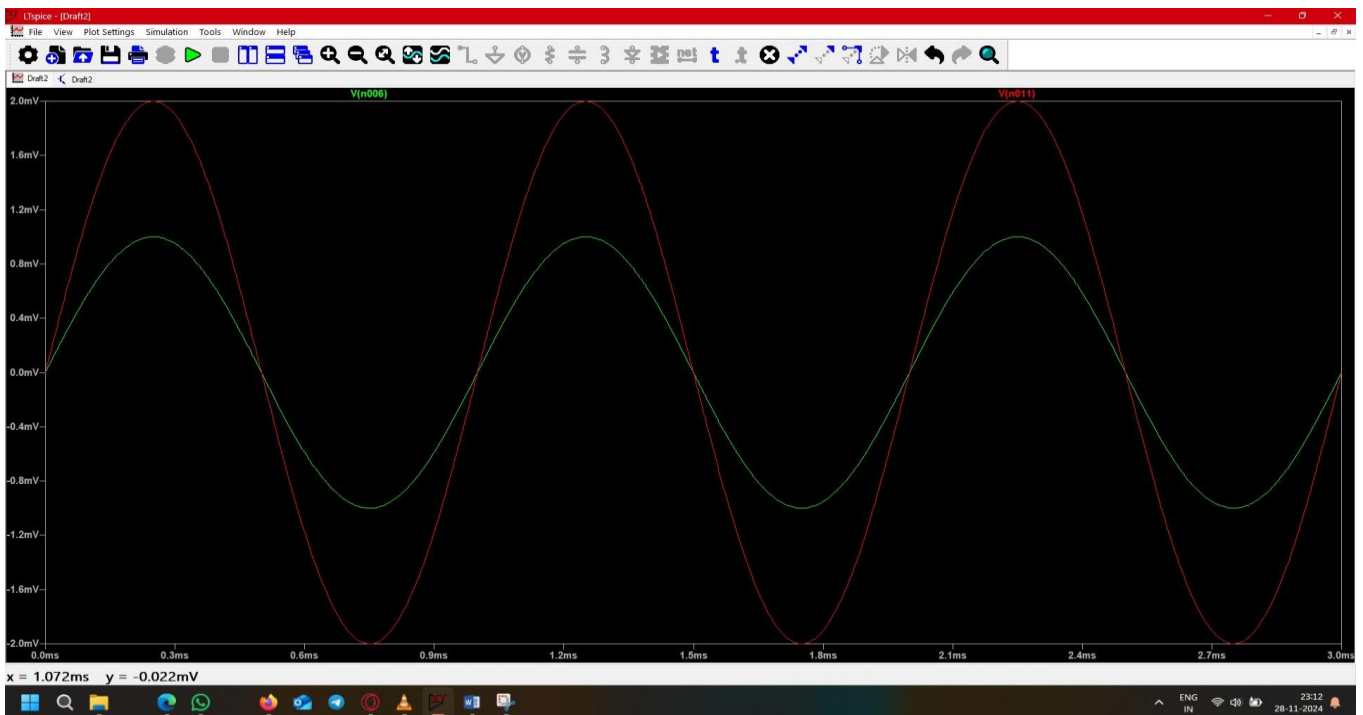

V_{out}: Wave Form

